

Lab 3 Report: Keypad Scanner

1 Introduction

In this lab, I created an interface between a keypad and the dual-display system developed in Lab 2. When a number is pressed on the key pad, the number is recorded on the 2 displays. The most recently pressed number is shown on the "right" display (closer to the bottom of the board). The second most recently pressed number is shown on the "left" display (close to the top of the board). If no buttons have been pressed, the displays initialize at 0. Figure 1 illustrates an example where "42" was entered into the keypad.

 


Figure 1: The latest number entered on the keypad is displayed on the bottom display. The second latest number is displayed on the top.

2 Design and Testing Methodology

2.1 Hardware

The keypad has 4 rows and 4 columns, which allows me to represent all 16 hex values (see Figure 2). When a particular button is pressed its row and column are connected. For example, the button for the number 5 is on row 1 and column 1. When that button is pressed, row 1 and col 1 will be in contact. If pin R1 was pulled to HIGH, pin C1 would also register a HIGH.

To detect which button is pressed, first each row is powered individually. Then the logic levels of the columns are read to determine if any buttons are pressed. Since the rows are being powered, they will always resolve to HIGH or LOW. However, to ensure that the columns also resolve to a logic level, pull-down resistors are placed on the column pins (C0 - C3). In this configuration, if a button is pressed, it will read HIGH, otherwise it will read low (See Figure 3). Pull-up resistors were not chosen because they would cause all the column pins to read HIGH regardless of whether or not its corresponding button is being pressed.

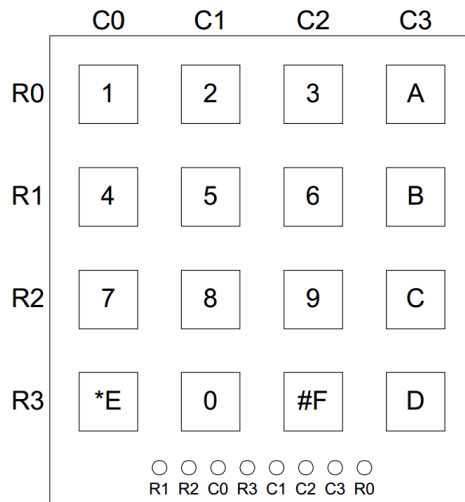


Figure 2: Pinout and key layout of the keypad. Image obtained from the HMC, E155 lab page.

2.2 Button Bounce

One of the challenges with using the keypad is a phenomenon known as "button bounce." This occurs because when a mechanical button is pressed and released, the button continues to move up and down for a short duration of time. This in turn causes the contact to close and open. Figures 4 and 5 show button bounce as viewed from an oscilloscope.

 


Figure 3: Schematic representation of the keypad. When a button is pressed, its row and col are connected.

 


Figure 4: Button bounce when the button is pressed down.

 


Figure 5: Button bounce when the button is released.

2.3 Software

The general approach to interpreting data from the keypad is as follows. First row 0 is powered. The column pins are read. If a button in that row is pressed down, the row remains powered until the button is released. If no button is pressed, row 0 is turned off and then row 1 is powered. Repeat. This finite state machine is shown in Figure 6. When button presses do occur, they are decoded based on the row being powered and the column that is read as HIGH. If multiple columns are HIGH at the same time, the left-most button is taken as the one being pressed down.

To cope with the challenge of button bounce, the control loop rate is run at a slow enough

frequency to avoid sampling twice in the same button press. This means that if the button is sampled while the signal is bouncing as in Figure 4, either a HIGH or LOW will be sampled. However, the next sample will be taken after the signal has resolved to a steady value. So, to the controller no bouncing in the signal is visible.

From Figures 5 and 4, I can see that longest observed button bounce duration is $340\mu s$. So, if only 1 row was kept HIGH, the fastest the columns should be sampled to avoid button bounce (and accounting for a factor of safety of 2) is once every $680\mu s$. Since there are 4 rows and I'm going to only sample the columns for a given row once every 4 samples, I can sample sequential rows at $\frac{680\mu s}{4} = 170\mu s$. This corresponds with a frequency of 5.8kHz.

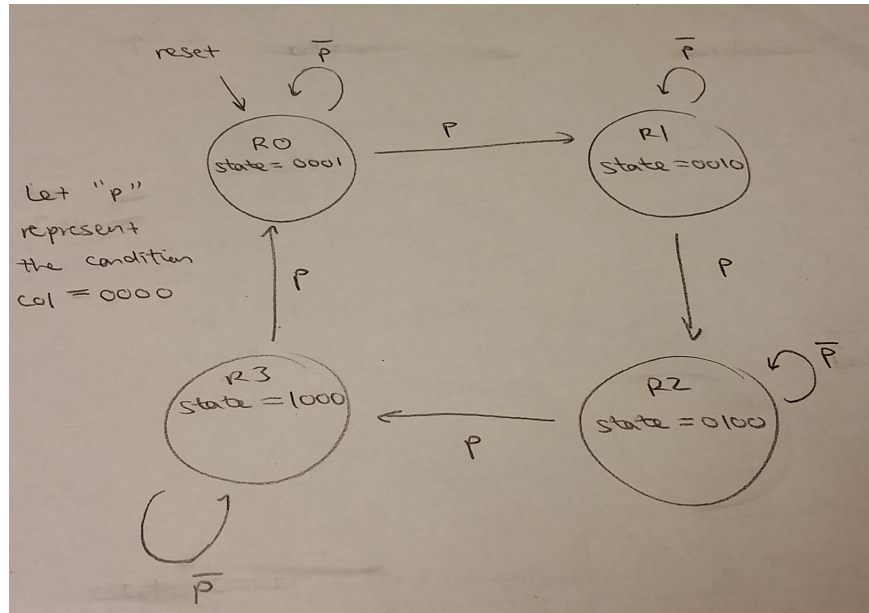


Figure 6: Finite state machine which keeps track of which row is being scanned.

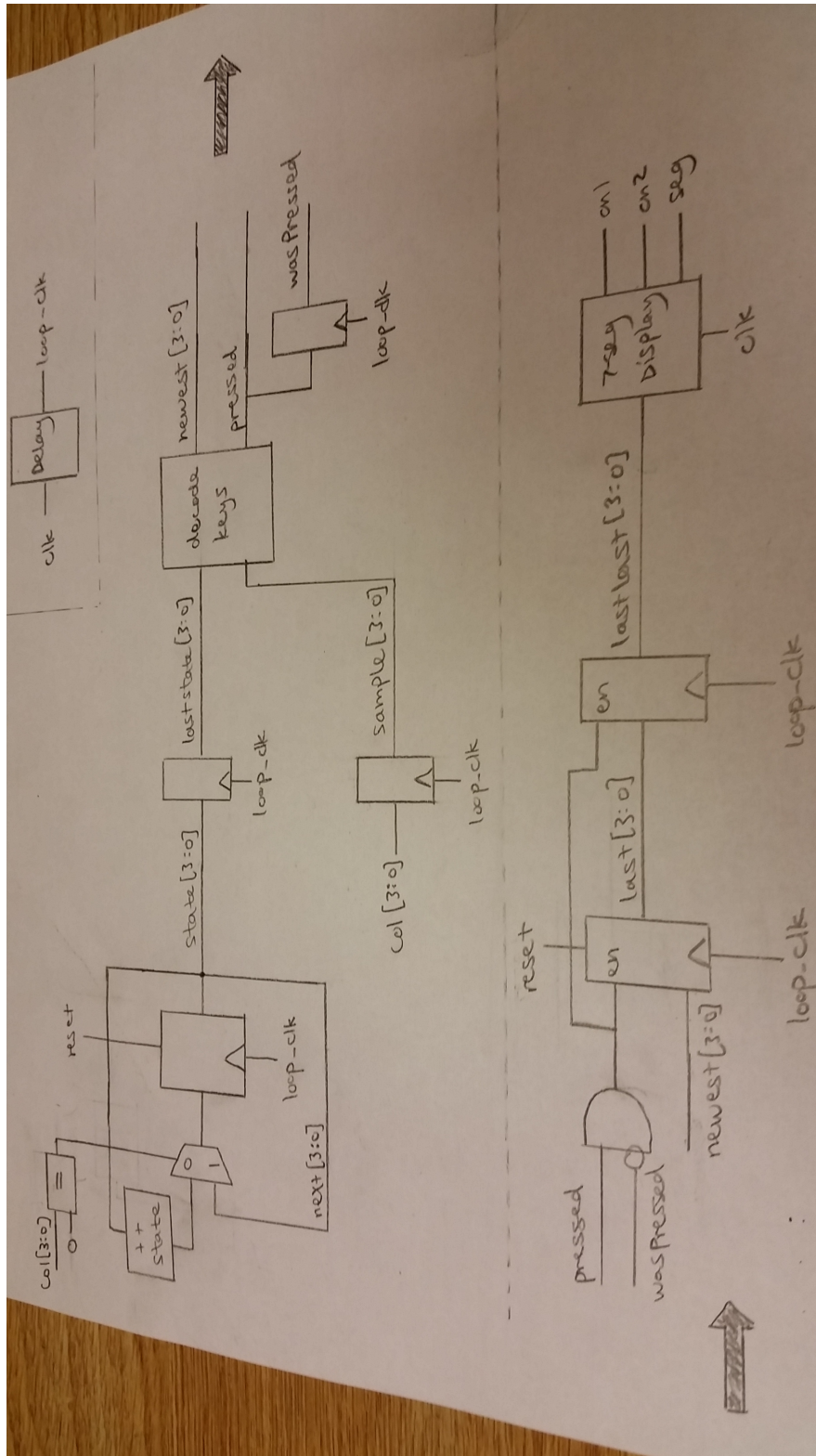


Figure 7: Control flow of the program.

2.3.1 Simulation

The code's logic was tested in ModelSim-Altera. The following show the results of the wave simulations that were run. The program was simulated in sections to ease debugging and wave simulation viewing.

 


Figure 8: To slow the sampling rate of the program, a "loop clk" was created to run at a slower rate than the on board clk. All flip-flops in the design are run based on this this slower clock signal. Note that the loop clock in actuality runs much slower than what is shown.

 


Figure 9: Even if the columns signal bounces, only one sample is taken. Bounce does not appear in the control signal "newest."

 


Figure 10: The keypad decoder works! The signal state[3:0] gives the row that's being powered and col[3:0] gives which row is being powered. The hex symbol is on the signal "newest."

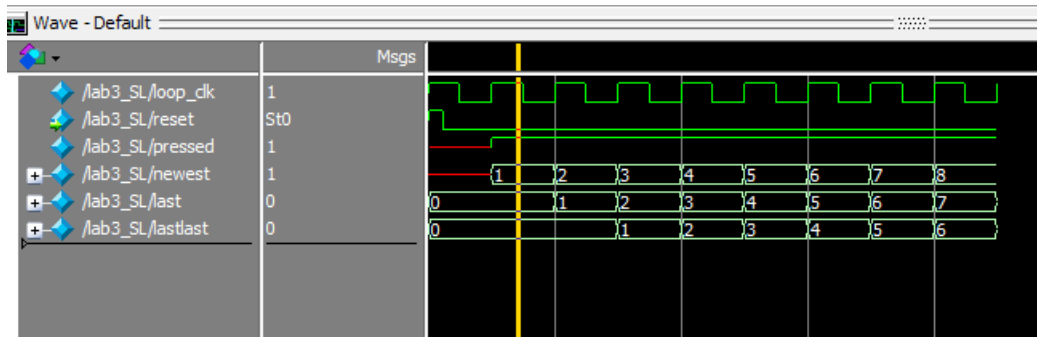


Figure 11: The program accurately remembers the last two numbers. "last" is the latest number entered. "lastlast" is the second to last number entered.



Figure 12: The main finite-state-machine keeps track of which row is being powered. The state uses 1-hot encoding so that it can be directly routed to the output. "next" represents the next state. When the reset signal is pulled high, the state resets synchronously to 0001.

 


Figure 13: When a button is pressed, the FSM is frozen in its current state. This prevents the program from registering a button that's being held down as multiple button presses.

3 Technical Documentation

The following section shows schematics for the breadboard circuit that was built. The source code is also provided.

3.1 7-Segment Decoder Truth Table

7-Segment Display Truth Table												
Inputs					Ouputs							
s3[3]	s3[2]	s3[1]	s3[0]	(hex)	G	F	E	D	C	B	A	(hex)
0	0	0	0	0x0	1	0	0	0	0	0	0	0x40
0	0	0	1	0x1	1	1	1	1	0	0	1	0x79
0	0	1	0	0x2	0	1	0	0	1	0	0	0x24
0	0	1	1	0x3	0	1	1	0	0	0	0	0x30
0	1	0	0	0x4	0	0	1	1	0	0	1	0x19
0	1	0	1	0x5	0	0	1	0	0	1	0	0x12
0	1	1	0	0x6	0	0	0	0	0	1	0	0x02
0	1	1	1	0x7	1	1	1	1	0	0	0	0x78
1	0	0	0	0x8	0	0	0	0	0	0	0	0x00
1	0	0	1	0x9	0	0	1	1	0	0	0	0x18
1	0	1	0	0xA	0	0	0	1	0	0	0	0x08
1	0	1	1	0xB	0	0	0	0	0	1	1	0x03
1	1	0	0	0xC	0	1	0	0	1	1	1	0x27
1	1	0	1	0xD	0	1	0	0	0	0	1	0x21
1	1	1	0	0xE	0	0	0	0	1	1	0	0x06
1	1	1	1	0xF	0	0	0	1	1	1	0	0x0E

Table 1: Truth table for 7-Segment LED decoder

3.2 7-segment Displays Schematic

 


Figure 14: Schematic for reset button.

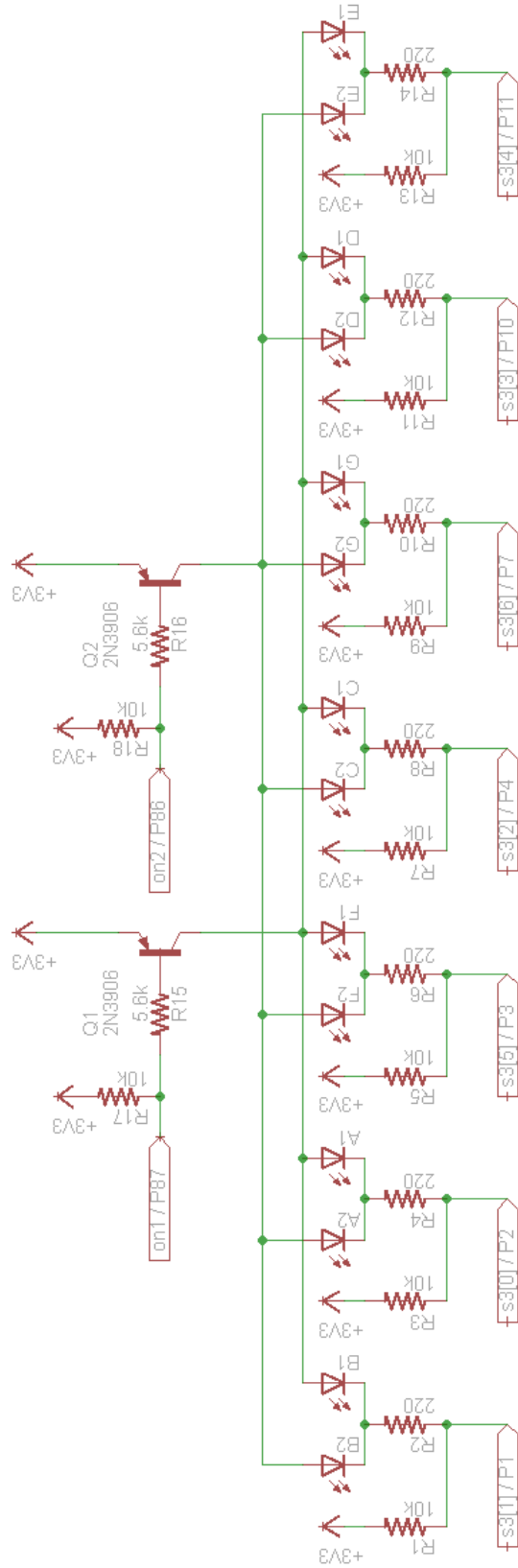


Figure 15: Full schematic for dual 7-segment display. Note that on1 and on2 toggle the two displays on and off. Only one or the other is on at any given time.

3.3 Pin Mapping

Keypad Pin Mapping - Rows			
R0 / state[0]	R1 / state[1]	R2 / state[2]	R3 / state[3]
P70	P66	P67	P69

Table 2: Pin mapping of keypad - Rows

Keypad Pin Mapping - Columns			
C0 / col[0]	C1 / col[1]	C2 / col[2]	C3 / col[3]
P68	P73	P72	P71

Table 3: Pin mapping of keypad

Control Signals Pin Mapping			
on1	on2	clk	reset
P87	P86	P88	P60

Table 4: Pin mapping of control signals

7 - Segment Display Pin Mapping						
seg[0]/A	seg[1]/B	seg[3]/C	seg[4]/D	seg[5]/E	seg[6]/F	seg[7]/G
P2	P1	P4	P10	P11	P3	P7

Table 5: Pin mapping of 7-segment display

3.4 System Verilog Code

3.4.1 Controller

```
1  /* This is the project wrapper that inits all the
2  individual components of the project
3
4  Author: Sherman Lam
5  Email: slam@g.hmc.edu
6  Date: Sep 25, 2014
7  */
8  module lab3_SL(    input logic clk, reset,
9                    input logic [3:0] col,
10                   output logic on1,on2,
11                   output logic [3:0] state,
12                   output logic [6:0] seg);
13    //wires
14    logic [3:0] newest;
15    logic [3:0] last;
16    logic [3:0] lastlast;
17    logic pressed;
18    logic wasPressed;
19    logic loop_clk;
20    logic [4:0] led;
21    logic [3:0] samples;
22    logic [3:0] laststate;
23
24    // run the clk at a slower rate
25    clk_sm          subClk( .clk(clk),
26                           .reset(reset),
27                           .loop_clk(loop_clk));
28
29    //keep track of the last 2 numbers
30    record_sm        memory( .loop_clk(loop_clk),
31                             .reset(reset),
32                             .pressed(pressed),
33                             .newest(newest),
34                             .last(last),
35                             .lastlast(lastlast),
36                             .wasPressed(wasPressed));
37
38    //fsm for deciding which row to check next
39    row_sm           row( .loop_clk(loop_clk),
40                         .reset(reset),
41                         .state(state),
42                         .col(col));
43
44    //sample the keys synchronously
45    sample_keys      sample( .loop_clk(loop_clk),
46                             .reset(reset),
47                             .col(col),
48                             .samples(samples));
49
50    //remember the last state
51    last_state       rememberState( .loop_clk(loop_clk),
52                                    .state(state),
53                                    .laststate(laststate));
54
55    //read the rows and cols of the keypad and decode to hex
```

```

56     decode_keys    read( .laststate(laststate),
57                          .samples(samples),
58                          .pressed(pressed),
59                          .newest(newest));
60
61     // keeps track if key was pressed in the last time step
62     record_pressed recordPressed( .loop_clk(loop_clk),
63                                   .reset(reset),
64                                   .pressed(pressed),
65                                   .wasPressed(wasPressed));
66
67     //seven segment display
68     seven_seg_displays seven_seg(.clk(clk),.reset(reset),.s1(lastlast),
69                                  .s2(last),.on1(on1),.on2(on2),.seg(seg),
70                                  .led(led));
71
72 endmodule
73
74
75 /* This keeps track of the last state
76
77 Author: Sherman Lam
78 Email: slam@g.hmc.edu
79 Date: Sep 27, 2014
80 */
81 module last_state(input logic loop_clk ,
82                  input logic [3:0] state ,
83                  output logic [3:0] laststate);
84     always_ff@(posedge loop_clk) begin
85         laststate <= state;
86     end
87 endmodule
88
89
90 /* This is a state machine that is used to keep
91 track of which row is being checked
92
93 Author: Sherman
94 Email: slam@g.hmc.edu
95 Date: Sep 25,2104
96 */
97 module row_sm( input logic loop_clk , reset ,
98               input logic [3:0] col ,
99               output logic [3:0] state);
100
101     //state encodings
102     parameter ROW1 = 4'b0001;
103     parameter ROW2 = 4'b0010;
104     parameter ROW3 = 4'b0100;
105     parameter ROW4 = 4'b1000;
106
107     //next state
108     logic [3:0] next;
109
110     always_ff@(posedge loop_clk) begin
111         if (reset)
112             state <= ROW1;
113         else if (col == 4'b0000) //only switch rows when button not pressed.
114             state <= next;

```

```

115         else
116             state <= state;
117
118     end
119
120     always_comb begin
121         //next state logic
122         case (state)
123             ROW1:      next = ROW2;
124             ROW2:      next = ROW3;
125             ROW3:      next = ROW4;
126             ROW4:      next = ROW1;
127             default:   next = ROW1;
128         endcase
129     end
130
131 endmodule
132
133
134 /* This samples the keys at the rising edge of loop_clk.
135 This is meant to prevent button bounce.
136
137 Author: Sherman Lam
138 Email: slam@g.hmc.edu
139 Date: Sep 26,2014
140 */
141 module sample_keys( input logic loop_clk , reset ,
142                    input logic [3:0] col ,
143                    output logic [3:0] samples);
144     always_ff@(posedge loop_clk) begin
145         if (reset)
146             samples <= 4'b0000;
147         else begin
148             samples <= col;
149         end
150     end
151 endmodule
152
153
154 /* This checks whether or not a button has been pressed.
155
156 Author: Sherman Lam
157 Email: slam@g.hmc.edu
158 Date: Sep 25, 2014
159 */
160 module decode_keys( input logic [3:0] laststate ,
161                    input logic [3:0] samples ,
162                    output logic pressed ,
163                    output logic [3:0] newest);
164     logic [4:0] key = 'b0;
165     always_comb begin
166         //check each row
167         case(laststate)
168             4'b0001: casez(samples) // find the first key
169                 4'b1???: key = 5'hA;
170                 4'b01??: key = 5'h3;
171                 4'b001?: key = 5'h2;
172                 4'b0001: key = 5'h1;
173                 default: key = 5'h10; // no key

```

```

174         endcase
175     4'b0010: casez(samples) // find the first key
176         4'b1???: key = 5'hB;
177         4'b01?: key = 5'h6;
178         4'b001?: key = 5'h5;
179         4'b0001: key = 5'h4;
180         default: key = 5'h10; // no key
181     endcase
182     4'b0100: casez(samples) // find the first key
183         4'b1???: key = 5'hC;
184         4'b01?: key = 5'h9;
185         4'b001?: key = 5'h8;
186         4'b0001: key = 5'h7;
187         default: key = 5'h10; // no key
188     endcase
189     4'b1000: casez(samples) // find the first key
190         4'b1?: key = 5'hD;
191         4'b01?: key = 5'hF;
192         4'b001?: key = 5'h0;
193         4'b0001: key = 5'hE;
194         default: key = 5'h10; // no key
195     endcase
196     default: key = 5'h10;
197 endcase
198
199 //key is only pressed if we found a key
200 pressed = ~key[4];
201 newest = key[3:0];
202
203 //TODO: change pressed to also depend on the state. Store pressed
204 // as a 4 bit number.
205
206 end
207 endmodule
208
209
210 /* This keeps track of whether or not a key was pressed in
211 the last time step
212
213 Author: Sherman Lam
214 Email: slam@g.hmc.edu
215 Date: Sep 25, 2014
216 */
217 module record_pressed( input logic pressed, loop_clk, reset,
218                       output logic wasPressed);
219     always_ff@(posedge loop_clk) begin
220         if (reset == 1'b1)
221             wasPressed = 1'b0;
222         else
223             wasPressed <= pressed;
224     end
225 endmodule
226
227
228
229 /* This is a state machine that sorts the presses
230
231 Author: Sherman Lam
232 Email: slam@g.hmc.edu

```



```

233 Date: Sep 27, 2014
234 */
235
236
237 /* This is the state machine that records the last
238 two values (last and lastlast) entered into the keypad.
239
240 Author: Sherman
241 Email: slam@g.hmc.edu
242 Date: Sep 25,2104
243 */
244 module record_sm( input logic loop_clk , reset ,
245                  input logic pressed , wasPressed ,
246                  input logic [3:0] newest ,
247                  output logic [3:0] last , lastlast );
248    // store
249    always_ff@(posedge loop_clk , posedge reset) begin
250        if (reset) begin
251            last = 'h0;
252            lastlast = 'h0;
253        end
254        //record only the first instance of the press
255        else if (pressed & (~wasPressed)) begin
256            lastlast <= last;
257            last <= newest;
258        end
259        else begin
260            lastlast <= lastlast;
261            last <= last;
262        end
263    end
264 endmodule
265
266
267 /* This is the state machine that outputs a slower
268 clk. This allows the program to run at a slower control
269 loop rate than that of the on board clock.
270
271 debounce math:
272 Scanning 1 row max: 2.9kHz
273 Scanning 1 row with FOS of 2: 1.45kHz
274 Scanning 4 rows: 5.8kHz
275 Loop every 6897 clock cycles
276 Toggle clk every 3448 clock cycles
277
278
279 Author: Sherman
280 Email: slam@g.hmc.edu
281 Date: Sep 25,2104
282 */
283 module clk_sm( input logic clk , reset ,
284               output logic loop_clk );
285
286 parameter HALF_PERIOD = 28'd3448; //5.9kHz loop rate
287 logic [27:0] counter = '0;
288
289 always_ff@(posedge clk , posedge reset) begin
290     if (reset == 1'b1) begin
291         counter = '0;

```

```

292     loop_clk = 0;
293 end
294 else if (counter >= HALF_PERIOD) begin
295     counter = '0;
296     loop_clk = ~loop_clk;      //toggle loop_clk
297 end
298 else begin
299     counter = counter + 1'b1;
300     loop_clk = loop_clk;
301 end
302 end
303
304
305 endmodule

```

3.4.2 7-segment display

```

1  /* This is the main module. It selects which set of switch
2  outputs to use and then decodes the number of the selected
3  switch. This also sets the clock that time-multiplexes the
4  two 7 segment outputs.
5
6  Author: Sherman Lam
7  Email: slam@g.hmc.edu
8  Date: Sep 17, 2014
9  */
10 module seven_seg_displays(input logic clk, reset,
11     input logic [3:0] s1,s2, //DIP switches
12     output logic on1, on2,   //if on1 is pulled LOW, LED set 1 is on.
13     output logic [6:0] seg,
14     output logic [4:0] led); //segment states
15
16     // time multiplexing
17     multiplexer ml(.clk(clk), .on1(on1), .reset(reset));
18
19     // the segments always have opposite states.
20     assign on2 = ~on1;
21
22     // select the right set of switches.
23     // on1 -> s1 is used. on2 -> s2 is used
24     // if on1 is pulled LOW, LED set 1 is on.
25     logic [3:0] s3;
26     assign s3 = on1? s2 : s1;
27
28     // 7 segment decoder
29     led7Decoder decoder(.s(s3), .seg(seg));
30
31     // sum the outputs and write to LED bar
32     assign led = s1 + s2;
33
34
35 endmodule
36
37
38 /* This module time multiplexes
39
40 Author: Sherman Lam
41 Email: slam@g.hmc.edu
42 Date: Sep 17, 2014

```

```

43 */
44 module multiplexer( input logic clk, reset,
45                     output logic on1);
46     // time multiplexer for switching between displays
47     logic [18:0] hPeriod = 19'd333333; // 120Hz toggling
48     logic [18:0] counter = 'b0;
49
50     always_ff @(posedge clk, posedge reset) begin
51         if (reset)
52             on1 = 1'b0;
53         else begin
54             if (counter >= hPeriod) begin
55                 counter = 'b0;
56                 on1 = ~on1;
57             end
58             else
59                 //on1 = on1;
60                 counter <= counter + 1'b1;
61         end
62     end
63
64 endmodule
65
66
67 /* This module decodes the switch inputs into an output for the
68    7 segment display on the development board.
69    s[3:0] = [sw3, ... ,sw1]
70    seg[6:0] = [g,f, ... ,b,a]
71
72    Author: Sherman
73    Email: slam@g.hmc.edu
74    Date: Sep 9, 2014
75 */
76 module led7Decoder( input logic [3:0] s, //4 DIP switches
77                    output logic [6:0] seg); //segments in 7-seg display
78
79     always_comb begin
80         //lookup table for s-seg relationship
81         case(s)
82             4'h0: seg = 7'b100_0000; // 0x0
83             4'h1: seg = 7'b111_1001; // 0x1
84             4'h2: seg = 7'b010_0100; // 0x2
85             4'h3: seg = 7'b011_0000; // 0x3
86             4'h4: seg = 7'b001_1001; // 0x4
87             4'h5: seg = 7'b001_0010; // 0x5
88             4'h6: seg = 7'b000_0010; // 0x6
89             4'h7: seg = 7'b111_1000; // 0x7
90             4'h8: seg = 7'b000_0000; // 0x8
91             4'h9: seg = 7'b001_1000; // 0x9
92             4'ha: seg = 7'b000_1000; // 0xA
93             4'hb: seg = 7'b000_0011; // 0xB
94             4'hc: seg = 7'b010_0111; // 0xC
95             4'hd: seg = 7'b010_0001; // 0xD
96             4'he: seg = 7'b000_0110; // 0xE
97             4'hf: seg = 7'b000_1110; // 0xF
98             default: seg = 7'b111_1110; // default to a dash
99         endcase
100
101     end

```

102 **endmodule**

4 Results and Discussion

The system works as expected and can handle rapid key sequences without freezing. If at any point the user desires to clear the numbers, a reset button is available that resets the displays to 0.

5 Conclusion

5.1 Time Spent

Programming, Simulating 13hrs

Breadboarding 0.5hrs

Writing Report 5hrs

Total Time Spent 18.5hrs

5.2 Suggestions for lab

None. Very challenging.