

Lab 1 Report: Utility Board Assembly

1 Introduction

This lab consisted of two main components:

1. Assembling the development board
2. Writing a simple program for interfacing LEDs and switches

In the first section of this lab, I assembled the E155 Utility Board from the provide kit. This board serves as a development board for a PIC32 microcontroller and a Cyclone III FPGA. The kit included basic through-hole components such as resistors, capacitors, switches, header pins, and LEDs. Other accessories included a VGA port, JTAG pins, and a jack for programming the PIC. The only surface-mount components were 3 voltage regulators (for 2.5V, 1.2V, and 3.3V). I ran some basic checks to verify that the board performed as expected. These checks included measuring the clock output and voltage regulator outputs.

In the second section of this lab, I used Quartus II to design an interface between the DIP switches on the development board LEDs. The LEDs included a LED bar on the development board and a 7-segment display that was wired off the board.

2 Design and Testing Methodology

2.1 Hardware

2.1.1 Development Board

The design of the development board was set by the course instructors and so it was simply assembled according to the provided lab instructions. As briefly mentioned in 1 several tests were run to verify that the hardware on the board functioned according to my expectations. The results included the following:

Pre-assembly Inspection No visible defects were found on the PCB or the components.

Using a multimeter, no short was detected across V_{in} and GND.

Power Supply When the board was powered by a 5V regulated input, the outputs of the voltage regulators read within 0.05V of the nominal voltage outputs.

Clock The output of the clock measured by an oscilloscope to be within 1MHz of the nominal frequency (40MHz).

LED Bar To check the LED bar's functionality, first the pin to one LED was connected (via a wire on the breadboard) to the pin of a switch. If the LED toggles with the switch, the LED was deemed functional. This test was repeated for all the LEDs. All LEDs performed as expected.

Switches To check the switches' functionality, first the pin to one LED on the LED bar was connected to the pin of one switch. If the LED toggles with the switch, the switch was deemed functional. This test was repeated for all the switches. All switches performed as expected.

2.1.2 7-Segment Display

In designing the 7-segment LED circuit, I aimed to make the circuit consistent and reliable. As seen in the Table 2.1.2, the control pins of the 7-segment LED were connected to pins 1,2,3,4,7,10, and 11. The layout of the segments on the display is shown in Figure 1.

7 - Segment Display Pin Mapping							
Pin	P2	P1	P4	P10	P11	P3	P7
Segment	A	B	C	D	E	F	G

Table 1: Pin Mapping from development board to 7-segment display

 


Figure 1: Segment ordering of a 7-segment display. Image from E155 Lab1.

In order to ensure that the logic on these pins either settled on LOW or HIGH, a pull up resistor was placed on the output of each pin. $10k\Omega$ was selected because it can pull the logic level of a pin to HIGH without drawing much current. In addition, each segment was wired in series with its own current limiting resistor. The value of this resistor was chosen to be 220Ω as determined by Equation 1. The schematic for a single segment of the display is shown in Figure 2. The full schematic for the 7-segment display is shown in Figure 5.

$$R = V/I = (V_{supply} - V_{diode})/I = (3.3V - 0.7V)/10mA = 260\Omega \approx 220\Omega \quad (1)$$

 


Figure 2: Schematic for segment B of the 7-segment display.

2.2 Software

7-Segment Display Truth Table												
Inputs					Outputs							
s[3]	s[2]	s[1]	s[0]	(hex)	G	F	E	D	C	B	A	(hex)
0	0	0	0	0x0	1	0	0	0	0	0	0	0x40
0	0	0	1	0x1	1	1	1	1	0	0	1	0x79
0	0	1	0	0x2	0	1	0	0	1	0	0	0x24
0	0	1	1	0x3	0	1	1	0	0	0	0	0x30
0	1	0	0	0x4	0	0	1	1	0	0	1	0x19
0	1	0	1	0x5	0	0	1	0	0	1	0	0x12
0	1	1	0	0x6	0	0	0	0	0	1	0	0x02
0	1	1	1	0x7	1	1	1	1	0	0	0	0x78
1	0	0	0	0x8	0	0	0	0	0	0	0	0x00
1	0	0	1	0x9	0	0	1	1	0	0	0	0x18
1	0	1	0	0xA	0	0	0	1	0	0	0	0x08
1	0	1	1	0xB	0	0	0	0	0	1	1	0x03
1	1	0	0	0xC	0	1	0	0	1	1	1	0x27
1	1	0	1	0xD	0	1	0	0	0	0	1	0x21
1	1	1	0	0xE	0	0	0	0	1	1	0	0x06
1	1	1	1	0xF	0	0	0	1	1	1	0	0x0E

Table 2: Truth table for 7-Segment LED decoder

The software was written for simplicity. In particular, there are two approaches to the decoder of the 7-segment display. Both approaches start with a truth table with the state of the switches (s[3:0]) as the inputs and the state of the led segments (led[6:0]) as the outputs (see Table 2). Note that since this is a common anode 7-segment display, pulling a pin LOW will actually turn on the corresponding segment. The first approach is to write the state of each segment in terms of the inputs (either sum-of-products or product-of-sums form). The second approach uses a case structure to implement a lookup table. Every possible value for s[3:0] is mapped to a value for led[6:0].

Quartus will theoretically optimize both approaches to similar (if not identical) logic blocks. So both will perform similarly in hardware. I chose to implement the lookup table since it is easier to code and less prone to coding mistakes. Also note that I configured the DIP switches with the LSB on the right (switch 4).

The decoder for the LED bar is similar to that of the 7-segment display. Its functionality is described in Figure 3.

In order to flash the LED at 2.4Hz, I setup a counter that tracks the number of clock cycles that have elapsed. To "flash" an LED, the LED must first be toggled on and then off. This requires two clock cycles. So, to flash the LED at 2.4Hz, the LED needs to be toggled at 4.8Hz, or every $\frac{40MHz}{4.8Hz} = 8333333$ cycles.

To check the logic output of my decoders, I simulated the module with ModelSim-Altera.

The results are shown in Figure 4.

S0	LED0	LED1
0	OFF	ON
1	ON	OFF

S1	LED2	LED3
0	OFF	ON
1	ON	OFF

S2	LED4	LED5
0	OFF	ON
1	ON	OFF

S3	S2	LED6
0	0	OFF
0	1	OFF
1	0	OFF
1	1	ON

LED7

Blink at ~2.4 Hz

Figure 3: Pin requirements for led bar decoder. Image from E155 Lab1.

 


Figure 4: Simulation output of the module with ModelSim-Altera.

3 Technical Documentation

3.1 System Verilog Code

```
/* This module is the wrapper for the project. It instantiates
   an instance of the led bar decoder and 7 segment decoder

   Author: Sherman Lam
   Email: slam@g.hmc.edu
   Date: Sep 9, 2014
*/

module lab1_SL( input logic clk,          //clock
                input logic [3:0] s,      //4 DIP switches
                output logic [7:0] led,    //8 lights on LED bar
                output logic [6:0] seg);   //segments in 7-seg display

    //instance of the led bar decoder
    ledBarDecoder bar(.clk(clk), .s(s), .led(led));
    //instance of 7-seg display decoder
    led7Decoder led7(.s(s), .seg(seg));

endmodule

/* This module decodes the switch inputs into an output for the
   color bar on development board.
   s[3:0] = [sw3, ... ,sw1]
   led[7:0] = [led7, ... ,led0]

   Author: Sherman Lam
   Email: slam@g.hmc.edu
   Date: Sep 9, 2014
*/
module ledBarDecoder(input logic clk,
                    input logic [3:0] s,
                    output logic [7:0] led);
    logic [23:0] count = 24'b0;
    logic [23:0] period = 24'h7F2815; //every 8333333 cycles of a 40MHz clock, the
                                      //7th led will toggle on or off. Yields a
                                      //flashing rate of 2.4Hz

    always_ff @(posedge clk) begin
        if (count >= period) begin
            count <= 24'b0;
            led[7] = ~led[7];
        end
        else
            count <= count + 1'b1;
    end

    always_comb begin
        led[1:0] = s[0] ? 2'b01 : 2'b10;
        led[3:2] = s[1] ? 2'b01 : 2'b10;
        led[5:4] = s[2] ? 2'b01 : 2'b10;
```

```

        led[6] = (s[3]&s[2]) ? 1'b1 : 1'b0;
    end

endmodule

/* This module decodes the switch inputs into an output for the
7 segment display on the development board.
s[3:0] = [sw3, ... ,sw1]
seg[6:0] = [g,f, ... ,b,a]

Author: Sherman Lam
Email: slam@g.hmc.edu
Date: Sep 9, 2014
*/
module led7Decoder( input logic [3:0] s, //4 DIP switches
                   output logic [6:0] seg); //segments in 7-seg display

    always_comb begin
        //lookup table for s-seg relationship
        case(s)
            4'h0: seg = 7'b100_0000; // 0x0
            4'h1: seg = 7'b111_1001; // 0x1
            4'h2: seg = 7'b010_0100; // 0x2
            4'h3: seg = 7'b011_0000; // 0x3
            4'h4: seg = 7'b001_1001; // 0x4
            4'h5: seg = 7'b001_0010; // 0x5
            4'h6: seg = 7'b000_0010; // 0x6
            4'h7: seg = 7'b111_1000; // 0x7
            4'h8: seg = 7'b000_0000; // 0x8
            4'h9: seg = 7'b001_1000; // 0x9
            4'ha: seg = 7'b000_1000; // 0xA
            4'hb: seg = 7'b000_0011; // 0xB
            4'hc: seg = 7'b010_0111; // 0xC
            4'hd: seg = 7'b010_0001; // 0xD
            4'he: seg = 7'b000_0110; // 0xE
            4'hf: seg = 7'b000_1110; // 0xF
            default: seg = 7'b111_1110; // default to a dash
        endcase
    end

endmodule

```

 


Figure 5: Schematic for full 7-segment display.

4 Results and Discussion

The program worked as expected. This indicates that the hardware (at least for the LEDs and switches) are all functioning. All aspects of the lab were completed, including simulation ModelSim and flashing the program to PROM.

5 Conclusions

Breakdown of time spent on lab:

Assembling Board 3.5hrs

Testing Hardware 0.5hrs

Programming, Simulating, Debugging 2hrs

Breadboarding 1hrs

Relearning Latex 1hrs

Writing Report 3hrs

Total Time Spent 11hrs